

Introduction to 3BA4-II

Dr. Andrew Butterfield

Timetable:

Monday, 1pm, H5

Tuesday, 10am, M17

Tuesday, 2pm, M20

Topic:

Integrated Circuit *Design*

Textbooks:

Weste & Eshraghian:

Principles of CMOS VLSI Design

Mead & Conway:

Introduction to VLSI Design

Web Page:

<http://www.cs.tcd.ie/Andrew.Butterfield/3BA4/>

CMOS

Complementary Metal-Oxide-Semiconductor

Two types of MOSFETs:

n-channel p-channel

△1

(many alternative notations)

△2

CMOS construction:

inputs feeding two networks

one pullup, connecting output to Power, with only p-type devices

one pulldown, connecting output to Ground, with only n-type devices

△3

Desired behaviour, for given inputs:

if we want 0 output,


produce path in pulldown network

if we want 1 output,


produce path in pullup network

3BA4—Part II: Lecture 1.2(CMOS)

 
△1 — We use the following symbols for n-channel and p-channel:



△2 — Alternative symbols are:

 

 △3 — The general structure of a CMOS circuit is:



Example CMOS Circuits

Behaviour of MOSFETS:

n-type: Logic '1' on gate, switch Closed

p-type: Logic '0' on gate, switch Closed

The Inverter:

a single p-type pullup MOSFET

a single n-type pulldown MOSFET

△1

Consider a more complex example:

$$\text{OUT} = \overline{A \cdot ((B \cdot C) + D)}$$


△2

What can single CMOS structures do ?


Function	Do-able ?
\overline{A}	yes
$\overline{A \cdot ((B \cdot C) + D)}$	yes
$A \cdot B$	no
$A \oplus B$	no
$A \cdot ((B \cdot C) + D)$	no
$\overline{A \cdot B}$	yes

3BA4—Part II: Lecture 1.3(Example CMOS Circuits)

△1 — A CMOS Inverter:

 

 △2 — The function $\overline{A \cdot ((B \cdot C) + D)}$:



Single Structure Functions

Single CMOS structures can implement functions of the form:
expression with only AND, OR and variables

Given a truth table, how do we establish if a function can be written like this ?

Consider the following functions as examples:

A	B	\overline{AB}	AB	$A \oplus B$
0	0	1	0	0
0	1	1	0	1
1	0	1	0	1
1	1	0	1	0

We can construct a *Hasse Diagram* for 2-inputs, showing the function \overline{AB} .

△1


We can build a single circuit if

- (i) bottom is labelled with (1) or ●
- (ii) bottom is labelled with (0) or ○
- (iii) any bottom-top path has labels which change only once, from (1) to (0)


△2,3,4

3BA4—Part II: Lecture 1.4(Single Structure Functions)

 
$\triangle 1$ — A fully labelled Hasse Diagram for \overline{AB} :



 
$\triangle 2$ — A compact Hasse Diagram for \overline{AB} :



 $\triangle 3$ — A compact Hasse Diagram for AB :



 $\triangle 4$ — A compact Hasse Diagram for $A \oplus B$:



Monotonic Bit-Functions

Consider the following ordering (\preceq)
on bit-strings of the same length (n):

$$a = a_{n-1}a_{n-2} \dots a_1a_0 \preceq b_{n-1}b_{n-2} \dots b_1b_0 = b$$

if b can be obtained from a
by changing zero or more 0s in a to 1s in b

if $a \preceq b$, then a will be connected to b
in a Hasse Diagram by zero or more arrows.

We say a function f is *monotonic decreasing* if

$$a \preceq b \implies f(a) \succeq f(b)$$

These are exactly the functions implementable as single CMOS structures

- (i) When all inputs are 0, all pulldowns are open, all pullups are closed, so output is 1.
- (ii) When all inputs are 1, all pulldowns are closed, all pullups are open, so output is 0.
- (iii) As we change 0s to 1s, we open pullups, and close pulldowns, so the only possible output transition is 1 to 0.

△1


△2

△3


3BA4—Part II: Lecture 1.5(Monotonic Bit-Functions)

Three diagrams illustrating CMOS structure behaviour.


$\triangle 1$ — All inputs 0:

 

$\triangle 2$ — All inputs 1:

 

 $\triangle 3$ — An input changing from 0 to 1:



Examples of 3-input functions

A Hasse diagram for $\overline{A(B+C)}$ shows that it is implementable as a single CMOS structure. $\triangle 1$

It also stresses the fact that \preceq is a *partial* order.

$$010 \not\preceq 101 \quad \text{and} \quad 101 \not\preceq 010$$

From a Hasse diagram for $A \oplus B \oplus C$ we find: $\triangle 2$


Every single-bit input change
causes output change.

EXOR is in some sense
the “most non-monotonic” bit function


EXOR is the most expensive gate to build
in CMOS, (or any other technology)

3BA4—Part II: Lecture 2.1(Examples of 3-input functions)

 $\triangle 1$ — Labelled Hasse diagram for $\overline{A(B+C)}$



 $\triangle 2$ — Compact Hasse diagram for $A \oplus B \oplus C$



Electronic Behaviour of MOSFETs

We consider an n-channel device to begin with.

Voltages: Drain-Source (v_{DS}), Gate-Source (v_{GS})

Currents: Drain-Source (i_{DS}), Gate (i_G)

$\triangle 1$

$$i_G = 0$$

How do we identify source and drain ?

The *more positive* is designated the *drain*.

$$v_{DS} \geq 0$$

Behaviour: $i_{DS} =$

$$\begin{aligned} &0, && \text{if } v_{GS} \leq V_{TN} \\ &\beta_N(v_{DS}(v_{GS} - V_{TN}) - v_{DS}^2/2), && \text{if } v_{GS} \geq V_{TN} \text{ and } v_{DS} \leq v_{GS} - V_{TN} \\ &\beta_N(v_{GS} - V_{TN})^2/2, && \text{or if } v_{DS} \geq v_{GS} - V_{TN} \end{aligned}$$


The important parameter is β_N , the MOSFET *transconductance*, as

$$i_{DS} \propto \beta_N$$

For p-channel devices, we multiply by (-1), and observe that the drain is the more *negative* terminal.

3BA4—Part II: Lecture 2.2(Electronic Behaviour of MOSFETs)

 △1 — A voltage and current-labelled diagram of an n-channel MOSFET



3BA4—Part II—Lecture 2.3 _____ © February 8, 2000 Andrew Butterfield

CMOS Inverter Characteristic

The *Transfer Characteristic* of an inverter maps v_{IN} to v_{OUT} :

△1

$$v_{OUT} = g(v_{IN})$$

We shall always assume: Power is 5V, $V_{TN} = +1V$, $V_{TP} = -1V$.

We assume also, to start, that $\beta_N = \beta_P$.

The shape of the transfer curve depends on the power voltage, V_{TN} , V_{TP} , and the *ratio* β_N/β_P △2

For an optimal speed and noise-immunity trade-off, we prefer to have $\beta_N/\beta_P = 1$


Usually, Power voltage, V_{TN} and V_{TP} are determined by manufacturer

Digital CMOS Designer's only concern is β_N/β_P !


(except for high performance — this gets hairy)

3BA4—Part II: Lecture 2.3(CMOS Inverter Characteristic)

 △1 — A CMOS inverter showing v_{IN} and v_{OUT}



△2 — A CMOS inverter transfer curve:

 

What Determines β_N and β_P ?

n-type MOSFET: Gate electrode, thin insulator p-type channel, between two n-type source/drain (s/d) regions.

Key Parameters:

L : Channel Length (along i_{DS} direction)
 W : Channel Width (across i_{DS} direction)
 t : Insulator Thickness
 ε_i : Insulator Permittivity
 μ : Charge Carrier Mobility

The transconductance is given by:

$$\beta = \mu \frac{\varepsilon_i}{t} \cdot \frac{W}{L} = \mu C_i \frac{W}{L}$$

where $C_i = \varepsilon_i/t$ is the capacitance/unit area of the gate.


Parameters ε_i , t and μ are fixed by manufacturer.

Parameters W and L are set by designer
(within limits)

One complication remains: $\mu_N \approx 3\mu_P$ (!)

3BA4—Part II: Lecture 2.4(What Determines β_N and β_P ?)

 $\triangle 1$ — An oblique sectioned view of an n-channel MOSFET:



3BA4—Part II—Lecture 3.1

© February 8, 2000 Andrew Butterfield

Compensating for $\beta_P \approx \beta_N/3$

We want $\beta_N = \beta_P$, where $\beta = \mu C_i W/L$,
but $\mu_N \approx 3\mu_P$ — we must compensate

In practice, devices have a minimum size
(circa $6\mu m$ in 1980, about $0.15\mu m$ in 1999).

Use current minimum size as unit of length
(sometimes called *lambda*, or λ)

Set all channel lengths to minimum ($L = 1$)
(this maximises gate switching speed)

Our balancing condition becomes:


$$\beta_N = \mu_N C_i W_N = \mu_P C_i W_P = \beta_P$$

We can only determine W_N , W_P as designers, so we get:

$$W_P = 3 \times W_N$$

3BA4—Part II: Lecture 3.1(Compensating for $\beta_P \approx \beta_N/3$)

 △1 — We show an Inverter labelled with correct sizes:



3BA4—Part II—Lecture 3.2 _____ © February 8, 2000 Andrew Butterfield

Effective Resistance Networks

Let us consider the example of a NAND gate △1

What is β for a network ?

The reciprocal of β is “effective resistance” R

$$R = 1/\beta \quad \beta \propto W \quad R \propto 1/W$$

This is approximate only, but works well enough

For a series connection, the resistance is the sum of the resistances of the components. △2


For a parallel connection, we might expect the rule for resistor in parallel to apply:

$$R = \frac{R_1 R_2}{R_1 + R_2}$$


However we find the parallel case is in one sense more complicated, while in another sense it becomes simpler !

3BA4—Part II: Lecture 3.2(Effective Resistance Networks)

△1 — Circuit Diagram for a NAND Gate

 

 △2 — Diagram showing series FETs viewed as equivalent Resistances



Handling Parallel Paths

Reminder: balancing β s to get symmetrical, fast changeover, with good noise properties.

NAND switches 0 to 1 in 2 distinct ways:

- (i) A single pullup has just closed
- (ii) both pullups have just closed

△1

Which case do we use for balancing ?

Worst Case: single branch working alone.

Analyse and consider parallel branches separately.


△2

Exploit symmetry:


- Two pullups are similar
- Two pulldowns are similar

3BA4—Part II: Lecture 3.3(Handling Parallel Paths)

 $\triangle 1$ — showing the distinction between one and both pullups acting to produce a 0 to 1 transition:



 $\triangle 2$ — showing the two branches needing balancing



Lets Calculate !

We assume co-efficient $\mu_N C_i = 1$ for simplicity

$$\beta_{PU} = \beta_P = W_P/3$$

$$\beta_{PD} = 1/R_{PD} \quad R_{PD} = 2R_N \quad R_N = 1/\beta_N$$

$$\beta_N = W_N$$

$$\Rightarrow R_N = 1/W_N$$

$$\Rightarrow R_{PD} = 2/W_N$$

$$\Rightarrow \beta_{PD} = W_N/2$$

We find that $W_N/2 = W_P/3$ to balance the gate

We have some freedom to choose what W_N and W_P are.

Two main possibilities:

Poss. 1 — let smallest have $W = 1$

$$W_N = 1 \quad W_P = 1.5$$

Poss. 2 — Choose smallest values keeping everything integral

$$W_N = 2 \quad W_P = 3$$

(often required by CAD tools)

3BA4—Part II: Lecture 3.4(Lets Calculate !)

3BA4—Part II—Lecture 3.5 _____ © February 8, 2000 Andrew Butterfield

A Simpler Way

There is a simple procedure that eliminates a lot of tedious error-prone algebra

△1

Step 1. Set all widths equal to 1

Step 2. Multiply all p-type widths by 3

Step 3.

For a series connection of length n ,
multiply all the widths by n .

Step 4.


Scale everything to minimise widths,
(subject to keeping them integral, if reqd.)

Notes:

- Steps 1 & 2 can be combined
- A MOSFET in several parallel paths is only multiplied once during Step 3.
- A MOSFET on several parallel paths of different lengths needs special treatment

3BA4—Part II: Lecture 3.5(A Simpler Way)

 △1 — showing complicated circuit sized the easier way



The sequence of 4 comma-separated numbers show the outcome of each of the four steps.

3BA4—Part II—Lecture 4.1 _____ © February 8, 2000 Andrew Butterfield

Manufacturing Process for ICs

Silicon (*Si*) — semiconductor (wanted very pure)

Sand(SiO_2) \rightarrow heat \rightarrow *Si*

Silicon Dioxide (SiO_2 , glass) - good insulator

Impurities (n-type, p-type) added
to control electronic behaviour

Pure *Si* arrives as tubular ingots

△1

Ingots sliced into *Wafers* (3 to 8 inches)

△2

Chip implemented as small rectangle (*Die*)
side dimensions typically a few mm.

△3


The Die is the “unit” of design.

Identical copies of Die tiled over wafer.


△4

3BA4—Part II: Lecture 4.1(Manufacturing Process for ICs)


$\triangle 1$ — of *Si* ingot:

 


$\triangle 2$ — of *Si* wafer:

 

$\triangle 3$ — of sample dies:

 

 $\triangle 4$ — of wafer tiled with dies:



IC Design Documents

Design “Documents” specify shapes on “Layers”.

Shapes on different layers overlap to make devices

A *Mask* is constructed per layer.

$\triangle 1$

Mask comprises opaque material on glass

— with some opaque material removed


$\triangle 2$

Masks cover entire wafer


Masks used to generate regions of desired shape — material determined by layer.

3BA4—Part II: Lecture 4.2(IC Design Documents)

 △1 — of document layers producing separate masks



△2 — of mask in cross-section

 

3BA4—Part II—Lecture 4.3 _____ © February 8, 2000 Andrew Butterfield

Patterning Steps

Using Mask to generate material regions:

1. Cover wafer with *Photo-Resist*
2. Expose photo-resist to light through mask
3. Develop photo-resist — exposed resist removed, unexposed resist remains
4. Process wafer to add/remove material
 - 4a — add (diffusion, sputter ...)

OR

- 4b — remove (etch ...)
5. Remove remaining resist

Variations

may apply material before Step 1
then etch in step 4b.


△1

△2


△3

3BA4—Part II: Lecture 4.3(Patterning Steps)


△1 — of state after Step 3.

 

△2 — of adding material in Step 4a

 

△3 — of removing material in Step 4b

 

3BA4—Part II—Lecture 4.4 © February 8, 2000 Andrew Butterfield

Producing an nMOS Device

Design uses 2 layers — *nDiff* and *Poly*

nDiff : n-type impurities diffused into wafer

Poly : Poly-crystalline Silicon used as wiring

Transistor constructed by crossing *nDiff* and *Poly*.

1. Cover wafer with thick SiO_2 (*Field Oxide*)

Why most ICs are built on silicon !!!

2. use *nDiff* mask to etch SiO_2 .

3a. Grow thin oxide layer (*Thinox*).

3b. Use *Poly* mask to pattern *Poly* and *Thinox*.

4. Diffuse n-type impurities into substrate

Self-Aligned Polysilicon-Gate Process

△1

△2

△3

△4


△5

△6


△7

3BA4—Part II: Lecture 4.4(Producing an nMOS Device)


△1 — of nMOS device layers:

 

 
△2 — of nMOS device and masks, with cross section lines indicated:



 
△3 — of wafer covered with oxide, also showing nice regular structure:



 
△4 — Cross sections of wafer after field oxide patterned by nDiff mask:



 
△5 — Cross sections of wafer after Poly/Thinnox patterned by Poly mask:



 △6 — Cross sections of wafer after n-type impurities are diffused:



 △7 — showing how it was done prior to self-aligned gate processes:



Mixing nMOS and pMOS

nMOS have n-type s/d regions in p-type substrate

pMOS have p-type s/d regions in n-type substrate

△1

How do we combine the two ?

One solution: Silicon on Sapphire (SOS)

Isolates devices, but expensive

△2

Cheaper solution:

build *Wells* of one substrate type in another.

nWell Technology:

p-type substrate

— n-channel devices built here

n-type well embedded into substrate

— p-channel devices built here


△3

Two new layers: nWell and pDiff


△4

3BA4—Part II: Lecture 5.1(TITLE)


△1 — of nMOS and pMOS in cross-section:

 


△2 — of nMOS and pMOS in SOS:

 

△3 — of nMOS and pMOS in nWell:

 

△4 — of new pDiff and nWell layers:

 

Connecting Devices

Poly and Diff act as wiring,
but cannot cross each other without making FETs.

Diff cannot cross nWell boundaries either

Need wiring layer — *Metal1*.

(often have Metal2,3, ... as well.)

Aluminium - layered on SiO_2 above Poly.

△1

It does not interact with lower layers
(with one exception, see later ...)

△2

How do we connect Metal to other layers ?


New “layer” called *CCut* (contact-cut)

Specifies where holes should be cut,
through *SiO₂*, to underlying layers.




3BA4—Part II: Lecture 5.2(Connecting Devices)


△1 — of Metal Layer:

 

 △2 — of Metal Layer passing over Poly and Diff:



△3 — showing CCut layer

 

3BA4—Part II—Lecture 5.3 _____ © February 8, 2000 Andrew Butterfield

Joining Metal to Poly/Diff

After Poly layer is done ...

- (i) Grow oxide over it
- (ii) Use CCut mask
to cut holes to underlying Poly or Diff
- (iii) place and pattern Metal1

△1

Contact Cut holes reach down to to Poly if below,
or else proceed to substrate surface.

Design Rules — “graphical syntax”

- (i) ensure design makes some sense
- (ii) ensure design can be reliably manufactured

A CCut Design Rule:

Never place CCut over Poly/Diff overlap (Gate)


Why ? Metal can spike through Poly

△2

Note: Metal1 may cross over Gate regions

3BA4—Part II: Lecture 5.3(Joining Metal to Poly/Diff)

$\triangle 1$ — of Metal-Poly contact

 

$\triangle 2$ — of Metal-Gate contact showing spiking

