

## 2BA4 RT Description of the Datapath

RW: R[DA]    If MD then  
                  FS(R[AA], if MB then R[BA]  
                  else Constant in)  
                  else DATA in,

$V \leftarrow C_n \wedge C_{n-1}$   
 $C \leftarrow C_n$   
 $Z \leftarrow R_{n-1}, R_{n-2}, \dots, R_0$   
 $N \leftarrow R_{n-1}$

## 2BA4 Symbolic Notation for Micro-ops

- ▶ Because human beings working in binary code tend to be highly error-prone, we usually employ intuitive symbols to specify datapath micro-ops.
- ▶ Typical **symbol/code** assignments are:

## 2BA4 Symbol-binary Map of Control Word Fields

DA, AA, BA	MB	FS	
Function Code	Function Code	Function	Code
R0 000	Register 0	G = A	00000
R1 001	Constant 1	G = A + 1	00001
R2 010		G = A + B	00010
R3 011	MD	G = A + B + 1	00011
R4 100	Function Code	G = A + B	00100
R5 101	Function 0	G = A + B + 1	00101
R6 110	Data In 1	G = A - 1	00110
R7 111		G = A	00111
	RW	G = A ∪ B	01000
	Function Code	G = A ∪ B	01010
	No Write 0	G = A - B	01100
	Write 1	G = A	01110
		G = B	10000
		G = sr B	10100
		G = sl B	11000

## 2BA4 Symbol Conversion

- ▶ With the symbolic notation it is easy to accurately specify control words which may then be automatically converted to binary.

▶ For example:  $R1 \leftarrow R2 + R3 + 1$

Field:	DA	AA	BA	MB	FS	MD	RW
Symbol:	R1	R2	R3		Register	F=A+B+1	Function Write
Binary:	001	010	011	0	00101	0	1

## 2BA4 Microoperations Example

- DIY - Convert these to binary and check your results against the table on the next slide.


Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 + \overline{R3} + 1$	R1	R2	R3	Register	$F = A + \overline{B} + 1$	Function	Write
$R4 \leftarrow \text{sl } R6$	R4	—	R6	Register	$F = \text{sl } B$	Function	Write
$R7 \leftarrow R7 + 1$	R7	R7	—	Register	$F = A + 1$	Function	Write
$R1 \leftarrow R0 + 2$	R1	R0	—	Constant	$F = A + B$	Function	Write
Data out $\leftarrow R3$	—	—	R3	Register	—	—	No Write
$R4 \leftarrow \text{Data in}$	R4	—	—	—	—	Data in	Write
$R5 \leftarrow 0$	R5	R0	R0	Register	$F = A \oplus B$	Function	Write

## 2BA4 Binary Control Words from Example

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	00101	0	1
$R4 \leftarrow \text{sl } R6$	100	000	110	0	11000	0	1
$R7 \leftarrow R7 + 1$	111	111	000	0	00001	0	1
$R1 \leftarrow R0 + 2$	001	000	000	1	00010	0	1
Data out $\leftarrow R3$	000	000	011	0	00000	0	0
$R4 \leftarrow \text{Data in}$	100	000	000	0	00000	1	1
$R5 \leftarrow 0$	101	000	000	0	01100	0	1
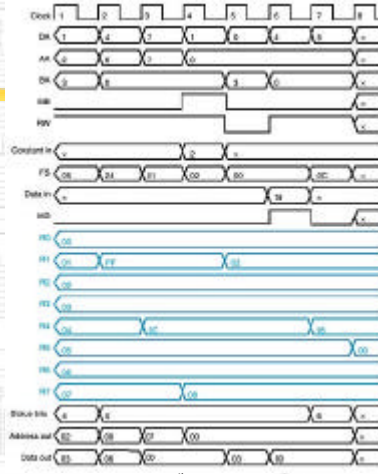
## 2BA4 Wave

- Examine the figure:
- Register transfer on Clock  $\uparrow$ .
- R0 - R7 are initialised to  $R_i \leftarrow i$ .




## 2BA4 Status Bits

- Status bits shows the input for the Zero, Negative, Carry-out and Overflow bits respectively.
- Hence the change following a control word change.
 
## Datapath Timing

- The total, worst case propagation delay determines the maximum rate at which we may clock a system.




Combinational logic  
with delay  $t_p$

Register with  
delay  $t_r$
 
## Timing

- For successful operations we must have:




$$T \geq t_p + t_r$$

$$T_{\min} = t_p + t_r$$

$$f_{\max} = 1 / T_{\min}$$

 
## Conventional and Pipelined Datapath timing

$$\begin{aligned} t_r &= 1\text{ns} \\ t_p &= 3+1+4+1+2\text{ns} \\ &= 11\text{ns} \\ T_{\min} &= 12\text{ns} \\ f_{\max} &= 1 / T_{\min} \\ &= 83.3\text{MHz} \end{aligned}$$


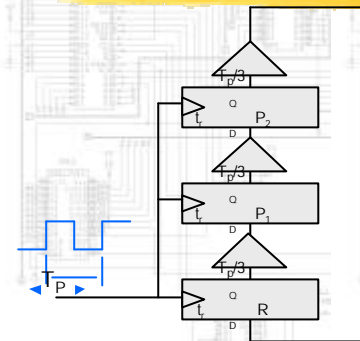
## Three-Stage Pipeline

- To speed things up we can introduce register into the combinational logic.



$$T_p \geq t_p/3 + t_r$$

$$T_{\max} = 1+4\text{ns}$$

$$\begin{aligned} f_{\max} &= 1 / T_{\max} \\ &= 200\text{MHz} \end{aligned}$$




## Pipelined Datapath

- ▶ When a datapath is pipelined it divides naturally into stages seen on the next slide.

- ▶ OF = Operand Fetch
- ▶ EX = Execute
- ▶ WB = Write Back



## Pipelined Datapath Schematic

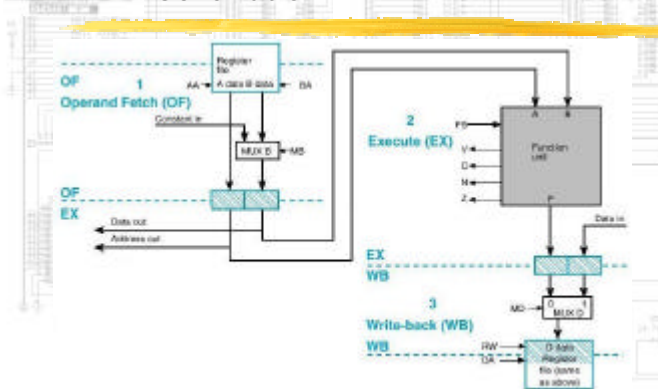

## Overlapped Execution

- ▶ This leads to overlapped execution of micro-ops, yielding an increased throughput.

- ▶ See next slide.
- ▶ DO PROBLEMS 25-29



## Pipe Execution Pattern

