



## Exercises:


Complete the following exercises and include the solutions with your report:

1. Using the circuit in the Figure 1, calculate

- § The current flowing in the circuit
- § The voltage drop across each resistor

2. Using the circuit in Figure 2, calculate the current flowing through each resistor in the circuit. What is the total current,  $I_T$ , flowing in the circuit?

**Figure 1**

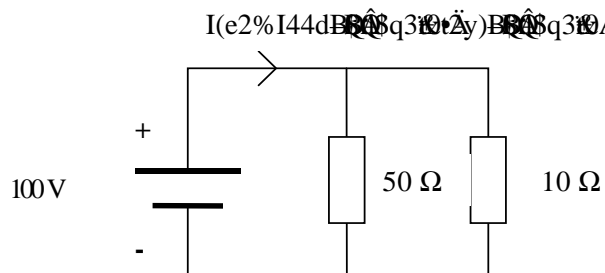

**Figure 2**

3. If the power dissipated in the  $10\Omega$  resistor of the circuit below is 20 watts. Determine

- The current in the  $10\Omega$  resistor
- The potential difference across XZ
-