 


- ▶ Synthesis produces a digital circuit that implements the behavior captured in the VHDL description.
- ▶ VHDL is also the bases for a simulation.
- ▶ Characteristics of digital systems:
 - ▶ Structural
 - ▶ Behavioral
 - ▶ Physical

Event, Propagation Delays and Concurrency



Signals



- ▶ May be 0, 1, or Z
- ▶ Equivalent to wires in digital circuits
- ▶ May be assigned values
- ▶ Signals are associated with time values
- ▶ Sequences of values determines the waveform
- ▶ Signal type depends on the level of abstraction
 - ▶ At gate level through wires (or, and, xor...)
 - ▶ At module level through integer (ALU...)

Shared Signals


- ▶ Hardware description languages must be expressive enough to describe signal that may be driven by one or more sources.
 - ▶ Bus

Design Entity

- ▶ Design entities could be:
 - ▶ Board
 - ▶ Chip
 - ▶ Gate
 - ▶ Transistor
- ▶ This design component behavior must be:
 - ▶ Described
 - ▶ Simulated

Design Entity - Gate Level Example

 - ▶ Half-Adder
 - ▶ Input signals: x, y
 - ▶ Output signals: sum, carry




Design Entity - Description

- ▶ Input signals
- ▶ Output signals
- ▶ Behavior
 - ▶ Truth table
 - ▶ Boolean equation
 - ▶ Wires between gates
- ▶ Two components in the design-entity description:
 - ▶ The interface
 - ▶ Internal behavior

Entity Declaration

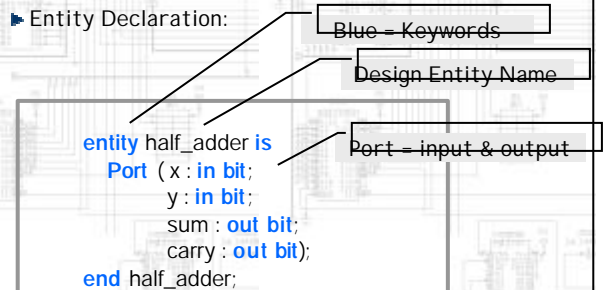- ▶ Interface to design entities through
 - ▶ Entity Declaration:



VHDL 2BA4 Declaration Details

- ▶ **Blue bold** type denotes VHDL reserved keywords (entity, port, ...)
- ▶ VHDL is not case sensitive
 - ▶ Half-adder = HALF-ADDER
- ▶ Ports define the input and output of the the design entity
- ▶ **Ports are signals** that enable communication between the design entity and other entities.
- ▶ Port signals must declare their types.

VHDL 2BA4 Port Declaration

- ▶ Signal types defined in the VHDL language
- ▶ **bit**
 - ▶ Represents a single-bit signal
- ▶ **bit_vector**
 - ▶ Represents a vector of signal of type **bit**
- ▶ Bit and bit_vector are only two out of several other VHDL data types.

VHDL 2BA4 IEEE 1164 Signals Values

IEEE 1164 standard defines nine-value signals:

U	Uninitialised
X	Forcing Unknown
0	Forcing 0
1	Forcing 1
Z	High Impedance
W	Weak Unknown
L	Weak 0
H	Weak 1
-	Don't Care

VHDL 2BA4 Library IEEE

The following modifications are required to make the previous entity declaration IEEE compliant.

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity half_adder is  
  Port ( x : in std_logic;  
        y : in std_logic;  
        sum : out std_logic;  
        carry : out std_logic);  
end half_adder;
```

2BA4 Signal Mode

► Port declaration distinguishes between:

- **in** - input signal
- **out** - output signal
- **inout** - bidirectional signal

Signal mode

```
entity half_adder is
  Port ( x : in std_logic;
```

2BA4 4 to 1 Multiplexer

This example uses std_logic_vector(7 downto 0);

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux is
  Port ( I0 : in std_logic_vector(7 downto 0);
        I1 : in std_logic_vector(7 downto 0);
        I2 : in std_logic_vector(7 downto 0);
        I3 : in std_logic_vector(7 downto 0);
        Sel : in std_logic_vector(1 downto 0);
        Z : out std_logic_vector(7 downto 0));
end mux;
```

Bit vector

2BA4 std_logic_vector(7 downto 0)

```
entity mux is
  Port ( I0 : in std_logic_vector(7 downto 0);
```

► This example refers to 8 bits long input vector.

- **bit 7** - most significant bit
- **bit 0** - least significant bit

2BA4 Entity's Internal Behavior

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity half_adder is
  Port ( x : in std_logic;
        y : in std_logic;
        sum : out std_logic;
        carry : out std_logic);
end half_adder;
```

```
architecture Behavioral of half_adder is
-- declaration
begin
-- description of behavior
end Behavioral;
```

VHDL describes the internal behavior in the architecture construct.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity half_adder is
  Port ( x,y: in std_logic;
         sum,carry : out std_logic);
end half_adder;

architecture concurrent_behavior of half_adder is
begin
  sun <= (x xor y) after 5 ns;
  carry <= (x and y) after 5 ns;
end concurrent_behavior;
```