

This could be the solution, but...


- ▶ Basic problem with solution 1:
 - ▶ Too much Hardware
 - ▶ Therefore an expensive design
 - ▶ The proposed design requires an AND gate for every input

Solution 2 – Multipurpose Pins


- ▶ Single pin with many functions
 - ▶ Electrical Implementation:
 - ▶ Tri-state
 - ▶ Bi-directional
 - ▶ Push and Pull
 - ▶ Open collector
 - ▶ Open drain
 - ▶ Wired-or
 - ▶ Wired-and

Ordinary Pins


- ▶ Pins, Pads and Wires.

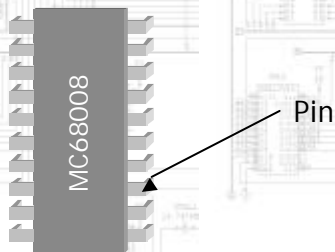


Integrated Circuit (IC)
Package

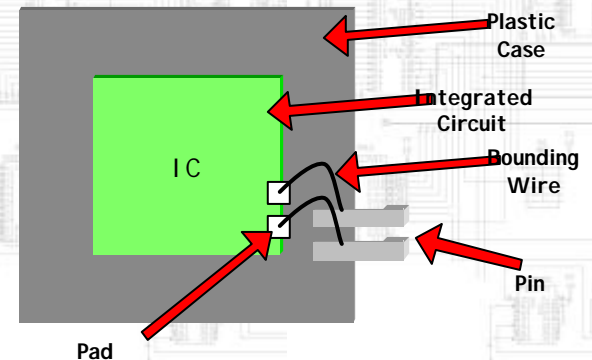


Integrated Circuit (IC) Package

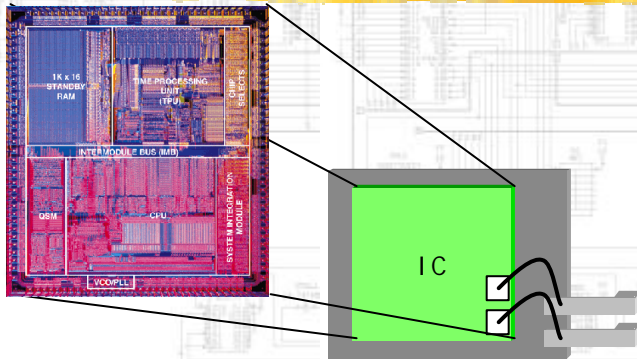3rd Lecture, M. Mancke, Page: 5

Input Pin

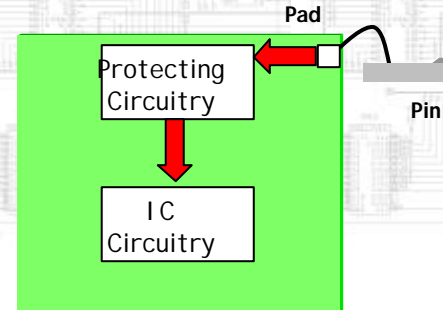3rd Lecture, M. Mancke, Page: 6

Output Pin

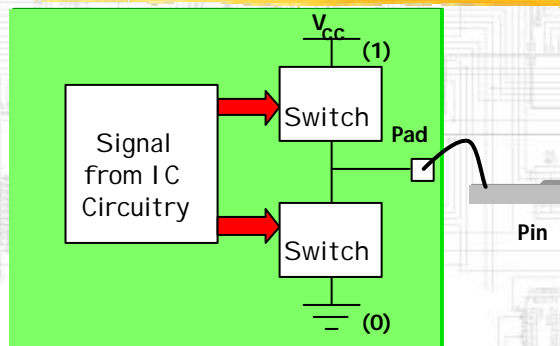
3rd Lecture, M. Mancke, Page: 7

Fully Driven Output Pin


- ▶ Fully Driven:
 - ▶ Always outputting (0) or (1).
 - ▶ Only one output per wire connection.
 - ▶ At any time, exactly one switch is open.

3rd Lecture, M. Mancke, Page: 8

Output (0)

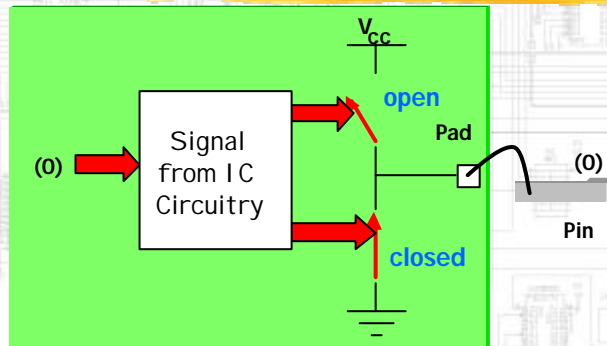


Output (1)

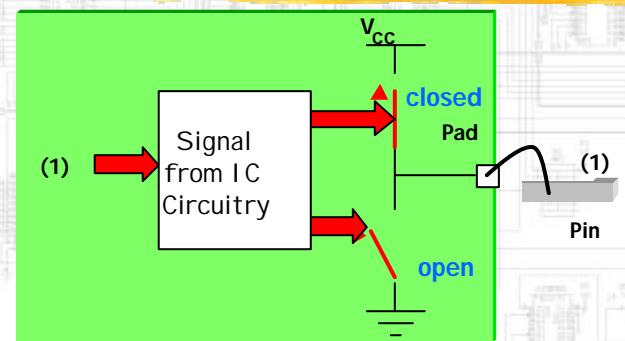

Tri-state Output

- ▶ Pin effectively has 3 states:
 - ▶ Low
 - ▶ High
 - ▶ High-Impedance (Hi-Z) [disconnected]
- ▶ Third state:
 - ▶ Can disconnect from wire.


Output (0), (1) or (Hi-Z)

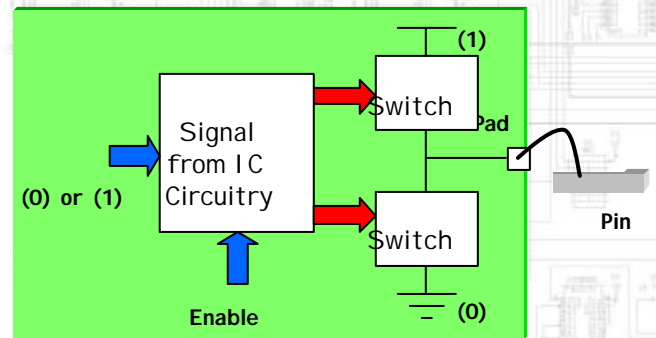


Disconnect (Hi-Z)

- ▶ To disconnect:
 - ▶ -> Open both switch
- ▶ At any time, at most one switch is closed.
- ▶ Both switches may be open.


High-Impedance (Hi-Z)

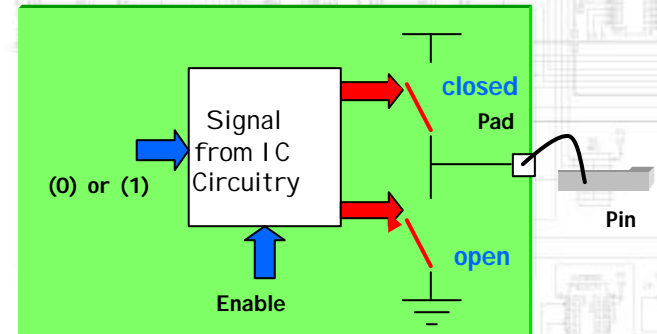


Tri-state - Pin Driving Conflict

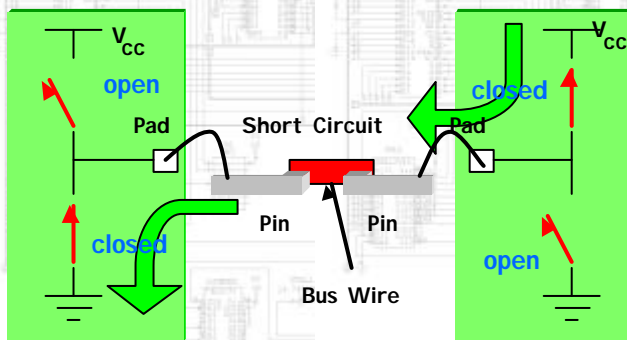

Need a Circuit Enable

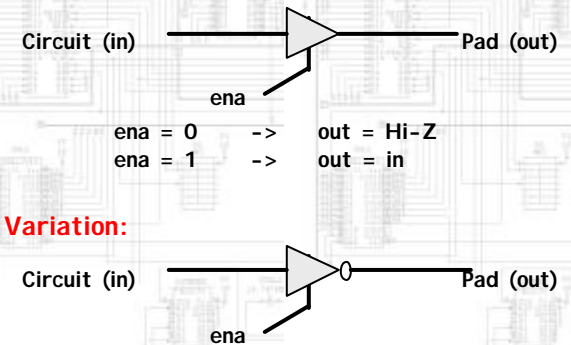

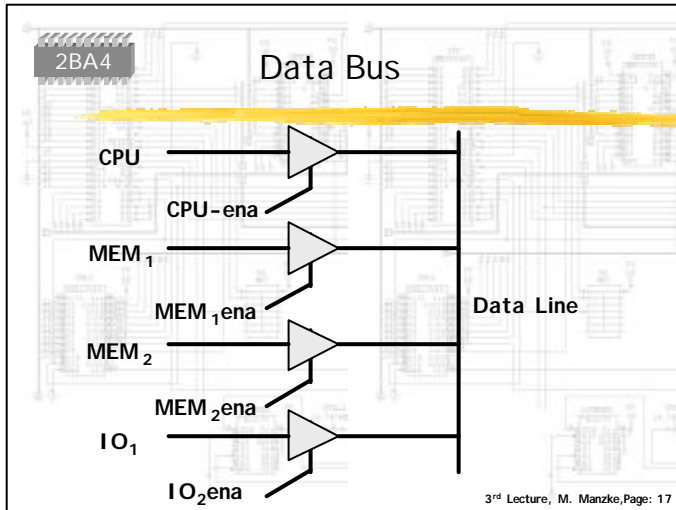

2BA4

Tri-state

- ▶ Cheap Hardware
- ▶ Need for Control Lines
- ▶ Design must ensure that only 1 control is active at a time.

3rd Lecture, M. Mancke, Page: 18

2BA4

Address, Data and Control Bus

- ▶ Address Bus
 - ▶ CPU → All Devices
- ▶ Data Bus
 - ▶ CPU ↔ All Devices
 - ▶ -> We need multiplexers
 - ▶ -> Tri-state

3rd Lecture, M. Mancke, Page: 19

