 


VHDL 2 to 4 Line Decoder

Structural



E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$\begin{aligned} D_0 &= E \bar{A}_1 \bar{A}_0 \\ D_1 &= E \bar{A}_1 A_0 \\ D_2 &= E A_1 \bar{A}_0 \\ D_3 &= E A_1 A_0 \end{aligned}$$

VHDL 2 to 4 Line Decoder (Page 1)

Structural

```
-- 2-to-4 Line Decoder: Structural VHDL Description
library ieee, lcd_vhdl;
use ieee.std_logic_1164.all, lcd_vhdl.func_prims.all;
entity decoder_2_to_4 is
    port(E, A0, A1: in std_logic;
         D0, D1, D2, D3: out std_logic);
end decoder_2_to_4;

architecture structural_1 of decoder_2_to_4 is

    component NOT1
        port(in1: in std_logic;
             out1: out std_logic);
    end component;
```


VHDL 2 to 4 Line Decoder (Page 3)

Structural

```
component NAND3
    port(in1, in2, in3: in std_logic;
         out1: out std_logic);
end component;

signal not_A0, not_A1: std_logic;
begin
    g0: NOT1 port map (in1 => A0, out1 => not_A0);
    g1: NOT1 port map (in1 => A1, out1 => not_A1);
    g2: NAND3 port map (in1 => not_A0, in2 => not_A1,
                       in3 => E, out1 => D0);
    g3: NAND3 port map (in1 => A0, in2 => not_A1,
                       in3 => E, out1 => D1);
    g4: NAND3 port map (in1 => not_A0, in2 => A1,
                       in3 => E, out1 => D2);
    g5: NAND3 port map (in1 => A0, in2 => A1,
                       in3 => E, out1 => D3);
end structural_1;
```

VHDL 4 to 1 Line Multiplexer

 

S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

2BA4 4 to 1 Line Multiplexer (Page 1)

```
-- 4-to-1 Line Multiplexer: Structural VHDL Description
library ieee, lcdl_vhdl;
use ieee.std_logic_1164.all, lcdl_vhdl.func_prims.all;
entity multiplexer_4_to_1_st is
  port(S: in std_logic_vector(0 to 1);
       D: in std_logic_vector(0 to 3);
       Y: out std_logic);
end multiplexer_4_to_1_st;

architecture structural_2 of multiplexer_4_to_1_st is
  component NOT1
    port(in1: in std_logic;
         out1: out std_logic);
  end component;
  component AND3
    port(in1, in2, in3: in std_logic;
         out1: out std_logic);
  end component;
```


2BA4 4 to 1 Line Multiplexer (Page 2)

```
component OR4
  port(in1, in2, in3, in4: in std_logic;
       out1: out std_logic);
end component;

signal not_S: std_logic_vector(0 to 1);
signal N: std_logic_vector(0 to 3);
begin
  g0: NOT1 portmap (S(0), not_S(0));
  g1: NOT1 portmap (S(1), not_S(1));
  g2: AND3 portmap (not_S(1), not_S(0), D(0), N(0));
  g3: AND3 portmap (not_S(1), S(0), D(1), N(1));
  g4: AND3 portmap (S(1), not_S(0), D(2), N(2));
  g5: AND3 portmap (S(1), S(0), D(3), N(3));
  g6: OR4 portmap (N(0), N(1), N(2), N(3), Y);
end structural_2;
```

2BA4 2 to 4 Line Decoder
Dataflow

Same as slide 1

 

E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

(b) Truth table

$$\begin{aligned} \bar{D}_0 &= \bar{E} \bar{A}_1 \bar{A}_0 \\ \bar{D}_1 &= \bar{E} \bar{A}_1 A_0 \\ \bar{D}_2 &= \bar{E} A_1 \bar{A}_0 \\ \bar{D}_3 &= \bar{E} A_1 A_0 \end{aligned}$$

2BA4 2 to 4 Line Decoder (Page 1)
Dataflow


```
-- 2-to-4 Line Decoder: Dataflow VHDL Description
library ieee, lcdl_vhdl;
use ieee.std_logic_1164.all, lcdl_vhdl.func_prims.all;
entity decoder_2_to_4 is
  port(E, A0, A1: in std_logic;
       D0, D1, D2, D3: out std_logic);
end decoder_2_to_4;

architecture dataflow_1 of decoder_2_to_4 is
  signal not_A0, not_A1: std_logic;
begin
  not_A0 <= not A0;
  not_A1 <= not A1;
  D0 <= not (not_A0 and not_A1 and E);
  D1 <= not (A0 and not_A1 and E);
  D2 <= not (not_A0 and A1 and E);
  D3 <= not (A0 and A1 and E);
end dataflow_1;
```

4 to 1 Line Multiplexer

Conditional DataFlow (When-Else)

Same as slide 4

 

4 to 1 Line Multiplexer (Page 1)

Conditional DataFlow (When-Else)

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_to_1_we is
    port (S : in std_logic_vector(1 downto 0);
          D : in std_logic_vector(3 downto 0);
          Y : out std_logic);
end multiplexer_4_to_1_we;

architecture function_table of multiplexer_4_to_1_we is
begin
    Y <= D(0) when S = "00" else
          D(1) when S = "01" else
          D(2) when S = "10" else
          D(3) when S = "11" else
          'X';
end function_table;
```

4 to 1 Line Multiplexer (Page 1)

Conditional DataFlow (With-Select)

```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_to_1_ws is
    port (S : in std_logic_vector(1 downto 0);
          D : in std_logic_vector(3 downto 0);
          Y : out std_logic);
end multiplexer_4_to_1_ws;

architecture function_table_ws of multiplexer_4_to_1_ws is
begin
    with S select
        Y <= D(0) when "00",
              D(1) when "01",
              D(2) when "10",
              D(3) when "11",
              'X' when others;
end function_table_ws;
```